

```

# CapTouch.py
# Starter code taken from https://learn.adafruit.com/adafruit-mp121-12-key-capacitive-touch-sensor-breakout-tutorial/python-circuitpython

import time
import board
import busio
# Import MPR121 module.
import adafruit_mpr121

from gpiozero import LED, LEDBoard

# Create I2C bus.
i2c = busio.I2C(board.SCL, board.SDA)

# Create MPR121 class.
mpr121 = adafruit_mpr121.MPR121(i2c)

# we will output touches on GPIO Pins of the Pi
TOUCH_LEFT = 12
TOUCH_DOWN = 16
TOUCH_UP = 20
TOUCH_RIGHT = 21

touchOut = LEDBoard(TOUCH_LEFT, TOUCH_DOWN, TOUCH_UP, TOUCH_RIGHT)

# Loop forever testing each input and printing when they're touched.
while True:
    print(mpr121[0].value, mpr121[2].value, mpr121[4].value, mpr121[6].value)
    touchOut.value = (mpr121[0].value, mpr121[2].value, mpr121[4].value, mpr121[6].value)

# sendSteps.py
from gpiozero import LED, LEDBoard
from time import *
from omxplayer.player import OMXPlayer
from pathlib import Path
from OneThing import *

STEP3 = 19
STEP2 = 13
STEP1 = 6
STEP0 = 5
BPM_CLK = 26
RESET_PIN = 17

stepLeds = LEDBoard(STEP3, STEP2, STEP1, STEP0)
bpmClockLed = LED(BPM_CLK)
resetLed = LED(RESET_PIN)

def sendSteps():
    # pulse reset signal before sending over steps
    resetLed.on()
    resetLed.off()
    # calculate sleep amount outside loop
    sleepAmount = 30/OneThingBPM
    # asynchronously play audio
    player = OMXPlayer(Path(OneThingMP3Path))
    # send over steps
    for step in OneThingSteps:
        start = time()
        stepLeds.value = tuple(step)
        # pulse BPM clock
        bpmClockLed.on()
        end = time()
        # sleep appropriately
        sleep(sleepAmount - (end - start))
        start = time()
        bpmClockLed.off()
        end = time()
        sleep(sleepAmount - (end - start))
    # make sure steps don't persist on led matrix
    stepLeds.value = tuple([0]*4)

# OneThing.py (Shortened for Purposes of Example)
OneThingBPM = 127.020
OneThingMP3Path = 'OneThing.mp3'
OneThingSteps = [
    [0,1,0,0],
    [0,0,0,0],
    [0,0,1,0],
    [0,0,0,0],
    [0,1,0,0]]

```

```

---SYSTEMVERILOG CODE---
//Top-level module - DDR.sv
module DDR(input logic clk,
           input logic bpmClk,
           input logic reset,
           input logic [3:0] step,
           input logic [3:0] button,
           output logic [3:0] colEnOut,
           output logic [7:0] col,
           output logic redLed,
           output logic greenLed,
           output logic [6:0] sevenSegDisplay,
           output logic leftDigitTransBase,
           output logic rightDigitTransBase);

    logic [15:0] counter;
    logic multiplexClk;
    logic [3:0] actionStep;
    logic [3:0] colEn;
    logic stepEn;

    always_ff@(posedge clk)
        if (reset) counter <= 0;
        else counter <= counter + 1;

    assign multiplexClk = counter[15];

    levelToPulse l2p(clk, reset, bpmClk, stepEn);
    colMuxer colMux(multiplexClk, reset, colEn);
    stepShiftRegister stepReg(clk, reset, stepEn, colEn, step, col, actionStep);

    assign colEnOut = ~colEn;

    logic [8:0] score;
    scoring scoring0(clk, reset, actionStep, stepEn, button, bpmClk, score, redLed, greenLed);

    scoreDisplay scoreDisplay0(clk, reset, score[8:0], leftDigitTransBase, rightDigitTransBase, sevenSegDisplay);

endmodule

// scoring.sv - Scoring algorithm determines if good/bad press and updates score and provides immediate feedback via green and red LEDs
module scoring(input logic clk,
              input logic reset,
              input logic [3:0] step,
              input logic beatEn,
              input logic [3:0] button,
              input logic bpmClk,
              output logic [8:0] score,
              output logic redLed,
              output logic greenLed);

    //INPUTS AND TIME CAPTURE
    logic [3:0] buttonPulse;
    levelToPulse l2p_0(clk, reset, button[0], buttonPulse[0]);
    levelToPulse l2p_1(clk, reset, button[1], buttonPulse[1]);
    levelToPulse l2p_2(clk, reset, button[2], buttonPulse[2]);
    levelToPulse l2p_3(clk, reset, button[3], buttonPulse[3]);

    logic [63:0] currentTime;
    logic [63:0] beatTime;
    always_ff @(posedge clk) begin
        if (reset) begin
            currentTime <= 0;
            beatTime <= 0;
        end
        else begin
            currentTime <= currentTime + 1;
            if (beatEn)
                beatTime <= currentTime;
        end
    end

    logic beatReset;
    //Beat is reset halfway between beatEnables
    levelToPulse l2p_4(clk, reset, ~bpmClk, beatReset);

    logic [3:0] buttonPressedDuringStep;
    always_ff @(posedge clk) begin
        if (reset || beatReset)
            buttonPressedDuringStep <= 0;
        else if (buttonPulse[0])
            buttonPressedDuringStep[0] <= 1;
    end
endmodule

```

```

        else if (buttonPulse[1])
            buttonPressedDuringStep[1] <= 1;
        else if (buttonPulse[2])
            buttonPressedDuringStep[2] <= 1;
        else if (buttonPulse[3])
            buttonPressedDuringStep[3] <= 1;
    end

    logic goodStep;
    assign goodStep = (step == buttonPressedDuringStep) && (step != 4'b0000);

    //CALCULATE SCORE
    logic addGoodStepToScore;
    logic deltaScore;
    always_ff @(posedge clk) begin
        if (reset) begin
            deltaScore <= 0;
            score <= 0;
        end
        else if (beatReset || deltaScore) begin //score as soon as step equals buttonPressedDuringStep
            deltaScore <= addGoodStepToScore;
            score <= score + deltaScore;
        end
    end
    assign addGoodStepToScore = goodStep && ~deltaScore;

    //LED FEEDBACK
    logic redLedEn;
    logic ledReset;
    logic stepExpected;
    always_ff @(posedge clk) begin
        if (ledReset)
            greenLed <= 0;
        else if (deltaScore)
            greenLed <= 1;
    end

    always_ff @(posedge clk) begin
        if (beatEn)
            redLed <= 0;
        else if (redLedEn)
            redLed <= 1;
    end

    assign stepExpected = (! step);
    assign redLedEn = (beatReset && !deltaScore && stepExpected && !goodStep);
    assign ledReset = (reset || beatReset);

endmodule

```

```

// stepShiftRegister.sv
module stepShiftRegister(input logic clk,

                        input logic reset,
                        input logic stepEn,
                        input logic [3:0] colEn,
                        input logic [3:0] inputStep,
                        output logic [7:0] col,
                        output logic [3:0] actionStep);

    logic [3:0] step0, step1, step2, step3, step4, step5, step6, step7;
    // shift register to shift steps every beat
    always_ff@(posedge clk)
        if (reset) begin
            step0 <= 4'h0;
            step1 <= 4'h0;
            step2 <= 4'h0;
            step3 <= 4'h0;
            step4 <= 4'h0;
            step5 <= 4'h0;
            step6 <= 4'h0;
            step7 <= 4'h0;
        end
        else if (stepEn) begin
            step0 <= inputStep;
            step1 <= step0;
            step2 <= step1;
            step3 <= step2;
            step4 <= step3;
            step5 <= step4;
            step6 <= step5;
            step7 <= step6;
        end

    assign actionStep = step7;
endmodule

```

```

always_comb
    case (colEn)
        4'b0001: col = {~step0[3], ~step1[3], ~step2[3], ~step3[3], ~step4[3], ~step5[3], ~step6[3], ~step7[3]};
        4'b0010: col = {~step0[2], ~step1[2], ~step2[2], ~step3[2], ~step4[2], ~step5[2], ~step6[2], ~step7[2]};
        4'b0100: col = {~step0[1], ~step1[1], ~step2[1], ~step3[1], ~step4[1], ~step5[1], ~step6[1], ~step7[1]};
        4'b1000: col = {~step0[0], ~step1[0], ~step2[0], ~step3[0], ~step4[0], ~step5[0], ~step6[0], ~step7[0]};
        default: col = {~step0[3], ~step1[3], ~step2[3], ~step3[3], ~step4[3], ~step5[3], ~step6[3], ~step7[3]};
    endcase

endmodule

// scoreDisplay.sv
module scoreDisplay(input logic clk, reset,
                    input logic [8:0] score,
                    output logic leftDigitTransBase, rightDigitTransBase,
                    output logic [6:0] seg);

    //Alternate LEDs at clk/(32768)=1220 Hz
    logic [16:0] counter; //16-bit counter
    logic switch; //LED group to drive (0 or 1)
    assign switch = counter[16]; //highest bit of counter
    always_ff @(posedge clk)
        counter <= counter + 1;
    //Only one transistor base low at a time
    assign leftDigitTransBase = switch;
    assign rightDigitTransBase = ~switch;
    //Switch to 7-segment display decoder
    logic [3:0] scoreHalf;
    assign scoreHalf = (switch ? score[7:4] : score[3:0]);
    hexto7seg dispDecoder(clk, scoreHalf, seg);
endmodule

//Module that decodes hexadecimal value to 7- segment display
module hexto7seg(input logic clk, input logic [3:0] hex, output logic [6:0] seg);
    //Common logic-high anode, output is cathode value
    //Logic-low output indicates turning segment
    always_comb begin
        case (hex)
            4'h0: seg <= 7'b1000000;
            4'h1: seg <= 7'b1111001;
            4'h2: seg <= 7'b0100100;
            4'h3: seg <= 7'b0110000;
            4'h4: seg <= 7'b0011001;
            4'h5: seg <= 7'b0010010;
            4'h6: seg <= 7'b0000010;
            4'h7: seg <= 7'b1111000;
            4'h8: seg <= 7'b0000000;
            4'h9: seg <= 7'b0011000;
            4'hA: seg <= 7'b0001000; //A
            4'hB: seg <= 7'b0000011; //b
            4'hC: seg <= 7'b1000110; //C
            4'hD: seg <= 7'b0100001; //d
            4'hE: seg <= 7'b0000110; //E
            4'hF: seg <= 7'b0001110; //F
        endcase
    end
endmodule

//levelToPulse.sv
module levelToPulse(input logic clk,
                    input logic reset,
                    input logic a,
                    output logic en);
    typedef enum {s0, s1, s2} StateType;

    StateType state;
    StateType nextState;

    always_ff@(posedge clk, posedge reset)
        if (reset) state <= s0;
        else state <= nextState;

    always_comb
        case(state)
            s0: nextState = a ? s1 : s0;
            s1: nextState = a ? s2 : s0;
            s2: nextState = a ? s2 : s0;
        endcase
endmodule

```

```

// emit pulse for one clk cycle
assign en = state == s1;
endmodule

// colMuxer.sv
module colMuxer(input logic multiplexClk,
                input logic reset,
                output logic [3:0] colEn);

    logic [3:0] nextColEn;

    always_ff@(posedge multiplexClk)
        if (reset) colEn <= 4'b0001;
        else      colEn <= nextColEn;

    always_comb
        case (colEn)
            4'b0001: nextColEn <= 4'b0010;
            4'b0010: nextColEn <= 4'b0100;
            4'b0100: nextColEn <= 4'b1000;
            4'b1000: nextColEn <= 4'b0001;
            default: nextColEn <= 4'b0001;
        endcase

endmodule

```